



**Faculty of Engineering & Technology**  
**Electrical & Computer Engineering Department**

**Advanced Digital System Design ENCS3310**

## **Project Report**

---

**Prepared by:**

Baraa Nasar                      1210880

**Instructor:** Dr. Abdallatif Abuissa

**Section:** 1

**Date:** 28-8-2023

## ABSTRACT

This report outlines the design and implementation of a Moore Finite State Machine (FSM) for a sequence detector. The detector is programmed to identify the specific sequence "1011". The project involves constructing a structured circuit that combines T-Flip Flops and combination logic to accurately detect the given sequence. An additional asynchronous reset input is incorporated to enable the resetting of the circuit.

The primary objective of this project is to develop a functional sequence detector that efficiently recognizes the pattern "1011" within input data streams. The detector's operation is based on a Moore FSM architecture, where the state transitions are governed by the input signals and the current state. The implemented design is subjected to rigorous testing using a comprehensive testbench. This testbench is used to validate the functionality of the detector, ensuring that it reliably identifies the sequence "1011" and produces the desired outputs.

The report underscores the significance of reliable sequence detection in various applications such as data analysis, error checking, and communication protocols. The successful realization and testing of the Moore FSM sequence detector demonstrate its effectiveness in accurately identifying the specified pattern. By comparing the circuit's behavior with its behavioral description, the report provides conclusive evidence of the design's accuracy and reliability.

In conclusion, the developed Moore FSM sequence detector offers a valuable solution for detecting the sequence "1011" in data streams. Its ability to function accurately, coupled with its flexibility for integration into various systems, highlights its potential applicability in a multitude of domains.

## Table of Contents

ABSTRACT .....	1
List of Figures .....	3
List of Tables .....	4
Brief introduction and background .....	5
Design philosophy .....	6
Step 1: Develop the state diagram .....	6
Step 2: Make Present State/Next State table .....	7
Step 3: Draw K-maps for TA, TB, TC and output (Y) : .....	8
Step 4:T-flip flop module.....	10
4.1: Block Diagram of T-flip flop .....	10
4.2: Truth Table of T-flip flop.....	10
4.3:T-Flip Flop Verilog Code.....	11
4.4: T-Flip Flop Test bench .....	12
Step5: Build Structural circuit using T-Flip and combination logic .....	13
Step6: Build behavioural description of the circuit. ....	14
Step7: Build testanalyser module .....	17
Step8: Build testbench module: .....	18
Results .....	19
Conclusion and Future work.....	21
APPENDIX CODE : .....	22

## List of Figures

Figure 1: The state diagram of the Moore FSM for the "1011"sequence detector _____	6
Figure 2: Block Diagram of T-flip flop _____	10
Figure 3: T-Flip Flop Verilog Code _____	11
Figure 4: T-Flip Flop Testbench code _____	12
Figure 5: structural circuit using T-Flip Flops and combination logic code _____	13
Figure 6: behavioural description of the circuit code _____	15
Figure 7: testanalyser module code _____	17
Figure 8: testanalyser module _____	18
Figure 9: T-flip flop testbench simulation _____	19
Figure 10: T-flip flop testbench result _____	19
Figure 11: testbench module simulation _____	20
Figure 12: testbench module result _____	20

## List of Tables

Table 1: State table of the Moore FSM for the "1011"sequence detector	7
Table 2: The K-maps for TA	8
Table 3: The K-maps for TC	8
Table 4: The K-maps for output Y	9
Table 5: The K-maps for TB	9
Table 6: Truth Table of T-flip flop	10

## Brief introduction and background

The aim of this project is to design a Moore Finite State Machine (FSM) for a sequence detector capable of recognizing the pattern "1011". A sequence detector is a fundamental component in digital circuit design and finds applications in various fields, including telecommunications, data processing, and control systems.

The task involves creating a structural circuit using T-Flip Flops and combinational logic to accurately detect the "1011" pattern. Detecting such sequences is crucial in larger digital systems, where the circuit can appropriately respond when specific data patterns are found.

In addition to circuit design, a comprehensive testing station will be developed to rigorously verify the design's functionality. This station will execute a series of test cases, comparing the actual circuit outputs to the expected results, identifying any discrepancies or errors, and addressing them.

Furthermore, to ensure the circuit's robustness and reliability, an asynchronous reset input will be included. This input allows for an immediate circuit reset when needed, preventing unexpected behavior.

In conclusion, this project aims to design a Moore FSM sequence detector for the "1011" pattern using T-Flip Flops and combinational logic. The subsequent verification and testing phases will ensure the circuit operates accurately and reliably, paving the way for its integration into larger and more complex digital systems.

## Design philosophy

### Step 1: Develop the state diagram

First, in step1, I'm designing a "1011" overlapping sequence detector, using Moore Model in Verilog. The Moore FSM keeps detecting a binary sequence from a digital input and the output of the FSM goes high only when a "1011" sequence is detected. The state diagram of the Moore FSM for the sequence detector is as shown below:

 


Figure 1: The state diagram of the Moore FSM for the "1011" sequence detector

The state diagram is a graphical representation of the logical circuit designed using T-Flip Flops to detect the sequence "1011." This state diagram illustrates how states transition between different states based on the input signals and represents the sequence detection process.

Let's explain the state diagram for this circuit:

1. **State 0 (S0):** This is the initial state of the circuit. When the circuit starts or when a reset signal is applied, it enters this state. In this state, the **sequence\_detected** output is disabled, and its value is 0.
2. **State 1 (S1):** If the current state is S0 and the **data\_in** signal has a value of 1, the circuit transitions to state S1. In this state, **sequence\_detected** is disabled, and its value is 0.
3. **State 2 (S2):** If the current state is S1 and the **data\_in** signal has a value of 0, the circuit transitions to state S2. In this state, **sequence\_detected** is disabled, and its value is 0.
4. **State 3 (S3):** If the current state is S2 and the **data\_in** signal has a value of 1, the circuit transitions to state S3. In this state, **sequence\_detected** is disabled, and its value is 0.

5. **State 4 (S4):** If the current state is S3 and the **data\_in** signal has a value of 1, the circuit transitions to state S4. In this state, **sequence\_detected** is activated, and its value becomes 1, indicating the detection of the "1011" sequence.

This state diagram illustrates how the circuit is configured and how states transition between T-Flip Flop units based on the input signals, which represent the received data.

## Step 2: Make Present State/Next State table

We'll use T-Flip Flops for design purposes.

Present State			Input	Next State			Output	Flip-Flop Excitations		
A	B	C	X	A	B	C	Y	TA	TB	TC
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	0	1
0	0	1	0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0	0	0	0
0	1	0	0	0	0	0	0	0	1	0
0	1	0	1	0	1	1	0	0	0	1
0	1	1	0	0	1	0	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1
1	0	0	0	0	1	0	1	1	1	0
1	0	0	1	0	0	1	1	1	0	1

Table 1: State table of the Moore FSM for the "1011" sequence detector



**Step 3: Draw K-maps for TA, TB, TC and output (Y) :**

AB \ CX	00	01	11	10
00				
01			1	
11	X	X	X	X
10	1	1	X	X

$T_A = A + BCX$

Table 2: The K-maps for TA

>>  $TA = A + B \& CX$

AB \ CX	00	01	11	10
00		1		1
01		1	1	1
11	X	X	X	X
10		1	X	X

$TC = AB + \bar{C}X + C\bar{X} + BCX$

Table 3: The K-maps for TC

>>  $TC = AB + C^{\wedge}X + BCX$

$\backslash Cx$	00	01	11	10
AB				
00				
01				
11	X	X	X	X
10	1	1	X	X

$Y = A$

Table 4: The K-maps for output Y

>>  $Y = A$

$\backslash Cx$	00	01	11	10
AB				
00				1
01	1		1	
11	X	X	X	X
10	1		X	X

$\bar{B}\bar{C}\bar{X} \leftarrow$  (from 00, 01)  
 $\bar{B}C\bar{X} \rightarrow$  (from 01, 11)  
 $A\bar{X} \rightarrow$  (from 01, 10)  
 $\bar{B}C\bar{X} \rightarrow$  (from 10, 11)  
 $\bar{B}C\bar{X} \rightarrow$  (from 10, 10)

$TB = A\bar{X} + B\bar{C}X + \bar{B}\bar{C}\bar{X} + \bar{B}C\bar{X}$

Table 5: The K-maps for TB

>>  $TB = A \& \sim X + B \& C \& X + B \& \sim C \& \sim X + \sim B \& C \& \sim X$

#### Step 4: T-flip flop module

A T-Flip Flop (Toggle Flip Flop) is a type of flip-flop where the output toggles (changes its state) based on the value of the T (toggle) input.

##### 4.1: Block Diagram of T-flip flop

 


Figure 2: Block Diagram of T-flip flop

##### 4.2: Truth Table of T-flip flop

Clock	INPUT		OUTPUT	
	RESET	T	Q	Q'
X	LOW	X	0	1
HIGH	HIGH	0	No Change	
HIGH	HIGH	1	Toggle	
LOW	HIGH	X	No Change	

Table 6: Truth Table of T-flip flop

The Q and Q' represents the output states of the flip-flop. According to the table, based on the input the output changes its state. But, the important thing to consider is all these can occur only in the presence of the clock signal.

RESET: The RESET pin has to be active HIGH. All the pins will become inactive upon LOW at RESET pin. Hence, this pin always pulled up and can be pulled down only when needed.

#### 4.3:T-Flip Flop Verilog Code

This code represents a Verilog module for a T flip-flop. The flip-flop changes its output state based on the input signal T when a positive edge occurs in the clock signal. If the reset signal is low, the flip-flop's output is set to zero regardless of the T signal.

In summary, this module implements the fundamental behavior of a T flip-flop in Verilog.

```
1 //Baraa Nasar
2 //1210880
3 //Sec:1
4 //T flip-flop module
5 module T_flipflop(Q,T,clock,reset);
6     output Q;
7     input T,clock,reset;
8     reg Q;
9
10    always@(posedge clock or negedge reset)
11        if(~reset)
12            Q=1'b0;
13        else
14            Q=Q^T;
15 endmodule
16
```

Figure 3: T-Flip Flop Verilog Code

#### 4.4: T-Flip Flop Test bench

The TFF Testbench provides a comprehensive testing environment to validate the T-Flip Flop module's operation under various conditions. It enables designers to observe how the module responds to clock signals, input changes, and resets, ensuring that it functions correctly according to its design specifications. This simulation is a crucial step in the digital design verification process before moving to hardware implementation

```
17 //Baraa Nasar
18 //1210880
19 //Sec:1
20 //T flip-flop Testbench module
21 module TFF_Testbench;
22     reg clk, reset, T;
23     wire Q;
24
25     // Instantiate the T flip-flop module
26     T_flipflop dff(Q, T, clk, reset);
27
28     // Clock generation
29     always begin
30         #5 clk = ~clk;
31     end
32
33     // Initial block
34     initial begin
35         // Initialize signals
36         clk = 0;
37         reset = 0;
38         T = 0;
39
40         // Apply reset
41         reset = 1;
42         #10 reset = 0;
43
44         // Test 1: T = 0
45         #5 T = 0;
46
47         // Test 2: T = 1
48         #5 T = 1;
49
50         // End simulation
51         $finish;
52     end
53 endmodule
54
```

Figure 4: T-Flip Flop Testbench code

### Step5: Build Structural circuit using T-Flip and combination logic

I built a structural circuit using T-Flip Flops and combination logic, that detect the sequence 1011 by calling full adder module 3 times, and the input(reset, clock,input\_x) and output Y1 . I built it as shown below:

```
50
57 //Baraa Nasar
58 //1210880
59 //Sec:1
60 //structural circuit using T-Flip Flops
61 module SequenceDetector (
62     input  clock,
63     input  reset,
64     input  in_x,
65     output reg Y1
66 );
67     wire A,B,C,TA,TB,TC;
68
69
70     or(TA,A,(B&C&in_x)); //TA=A+BCX
71
72     or(TB,(A&~in_x),(B&~C&~in_x),(B&C&in_x),(~B&C&~in_x));
73
74     or(TC,(A&B),(C^in_x),(B&C&in_x)); //TC=AB+C^X+BCX
75
76
77     T_flipflop G1( A,TA,clock,reset);
78     T_flipflop G2( B,TB,clock,reset);
79     T_flipflop G3( C,TC,clock,reset);
80     assign Y1=A;
81
82 endmodule
```

Figure 5: structural circuit using T-Flip Flops and combination logic code

## Step6: Build behavioural description of the circuit.

I built behavioural description of the circuit. I built it as shown below:

```
85 //Baraa Nasar
86 //1210880
87 //Sec:1
88 //behavioural description of the circuit
89 module sqd_moore( output reg in_x, output reg clock, output reg reset, output reg Y);
90
91     initial begin
92         in_x =0;
93         clock =0;
94         #10ns reset =1;
95         #10ns in_x=1;
96         #20ns in_x=0;
97         #30ns in_x=1;
98         #40ns in_x=1;
99     end
100 initial begin
101 repeat (11)
102     #20ns clock=~clock;
103 end
104
105 parameter S0=3'b000,
106           S1=3'b001,
107           S2=3'b011,
108           S3=3'b010,
109           S4=3'b110;
110
111 reg[1:0] Prsent_state,Next_state;
112
113 always @(posedge clock or negedge reset)
114 begin
115     if(reset==0)
116         Prsent_state <= S0;
117     else
118         Prsent_state<=Next_state;
119 end
120 begin
121
122     always @(Prsent_state ,in_x)
123     begin
124         case (Prsent_state)
125             S0:begin
126                 if(in_x==1)
127                     Next_state <= S1;
128                 else
129                     Next_state <= S0;
130             end
131             S1:begin
132                 if(in_x==0)
133                     Next_state <=S2;
134                 else
135                     Next_state <=S1;
136             end
137         endcase
138     end
139 end
```

```

137
138
139
140
141
142
143
144
145
146
147
148
149
150
151
152
153
154
155
156
S2:begin
    if(in_x==0)
        Next_state <=S0;
    else
        Next_state <=S3;
    end
S3:begin
    if(in_x==0)
        Next_state <=S2;
    else
        Next_state <=S4;
    end
S4:begin
    if(in_x==0)
        Next_state <=S2;
    else
        Next_state <=S1;
    end
endcase
end

157
158
159
160
161
162
163
164
165
166
167
168
169
170
always @(Prsent_state)
begin
    case (Prsent_state)
    S0: Y<=0;
    S1: Y<=0;
    S2: Y<=0;
    S3: Y<=0;
    S4: Y<=1;
    endcase
end
end
endmodule

```

Figure 6: behavioural description of the circuit code

### Module Overview:

The `sqd\_moore` module is designed to implement a Moore Finite State Machine (FSM) for sequence detection. It aims to detect the specific sequence "1011" within a stream of binary input data. This module utilizes a clock signal, a reset signal, and an input signal (`in\_x`) to perform the sequence detection.



### Initialization:

The module begins with an initial block that sets the initial values for ``in_x``, ``clock``, and ``reset``. It also generates a clock signal with a specified clock period, simulating the passage of time within the module.

### State Definitions:

The module defines five distinct states, namely ``S0``, ``S1``, ``S2``, ``S3``, and ``S4``, to represent different phases or conditions of the sequence detection process.

### State Transition:

The module employs an ``always`` block sensitive to the rising edge of the clock signal or the falling edge of the reset signal to manage state transitions. When the reset signal is low, the FSM resets to the initial state ``S0``. Otherwise, it transitions to the next state (``Next_state``) based on the current state (``Present_state``) and the value of the input signal ``in_x``.

### State Transition Logic:

Within the ``always`` block, a ``case`` statement is used to determine the ``Next_state`` based on the current state and the value of ``in_x``. For example, if the current state is ``S0`` and ``in_x`` is equal to 1, the ``Next_state`` is set to ``S1``. This logic defines the sequence detection criteria.

### Output Generation:

The ``Y`` output represents the result of the sequence detection. It is set based on the current state. When the FSM is in state ``S4``, ``Y`` is set to 1, indicating that the target sequence "1011" has been detected. In all other states, ``Y`` is set to 0.

In summary, the ``sqd_moore`` module is designed as a Moore FSM for sequence detection. It tracks the state of the detection process, transitions between states based on inputs and predefined criteria, and provides an output signal ``Y`` to indicate whether the target sequence is detected or not.

## Step7: Build testanlyser module

```
172
173 //Baraa Nasar
174 //1210880
175 //Sec:1|
176 module testanlyser (clock, Y1 , Y);
177     input clock,Y1 , Y ;
178
179     always @(posedge clock) begin
180         if (Y1==Y)
181             $display("True");
182         else
183             $display("false");
184     end
185
186 endmodule
```

Figure 7: testanlyser module code

The "testanlyser" module is designed to verify the performance of the circuit by comparing the signals Y1 and Y along with the clock signal.

**1. Verification Purpose:** The main purpose of this module is to ensure that the output signal Y1, which is generated by the "SequenceDetector" module, matches the expected output Y based on the behavioral description of the circuit.

**2. Signal Comparison:** Inside this module, there is an "always" block that is sensitive to the rising edge (posedge) of the clock signal. This means that whenever the clock signal transitions from low to high, the block is activated.

**3. Comparison Logic:** Within the "always" block, there is logic that checks if the signals Y1 and Y match. If they match, it means that the circuit is behaving as expected, and the module displays "True" as the output.

**4. Verification Process:** During simulation, as the clock signal toggles, this module continuously compares Y1 and Y. If they are consistent, it confirms that the circuit's behavior matches the expected behavior, and it outputs "True." If there is a mismatch between Y1 and Y, it would output "False," indicating that there might be an issue in the circuit.

In summary, the "testanlyser" module serves as a verification tool to confirm that the circuit, particularly the "SequenceDetector" module, is functioning correctly based on the expected behavioral description. It does this by continuously comparing the actual output Y1 with the expected output Y whenever the clock signal rises. If they match, it signals that the circuit is working as intended.

## Step8: Build testbench module:

```
187
188 //Baraa Nasar
189 //1210880
190 //Sec:1|
191 module testbench ;
192
193     wire in_x,clock,reset;
194     reg Y1 , Y ;
195
196     sqd_moore t1(in_x,clock,reset,Y);
197
198     SequenceDetector t3(clock,reset,in_x,Y1);
199
200     testanalyser t2(clock, Y1 , Y);
201
202 endmodule
```

Figure 8: testanalyser module

### Module Overview:

**1. module testbench :** This module represents the main environment for testing the circuit. It is used to set up the testing scenario and connect with other modules.

**2. wire in\_x, clock, reset:** These wires are used to create input signals. In this case, they are used to create signals in\_x, clock, and reset.

**3. reg Y1, Y:** These variables represent the signals that will be used to monitor and analyze the results. `Y1` and `Y` are the variables used to verify the correctness of signals generated by the circuit.

**4. sqd\_moore t1(in\_x, clock, reset, Y):** This line creates the sqd\_moore module and connects it to the required input signals and timing signals.

**5. SequenceDetector t3(clock, reset, in\_x, Y1):** Here, the SequenceDetector module is created and connected to the same signals.

**6. testanalyser t2(clock, Y1, Y):** This module is created to monitor signals and verify the performance of the circuit. It will compare the signal `Y1` with `Y` and print "True" if they match correctly.

In summary, the testbench module sets up the necessary environment for circuit testing, generates input signals, monitors the signals generated by the circuit, and verifies that it is functioning correctly.

## Results

The test benches were designed and executed to verify the accuracy of the implemented special counter circuit. The results obtained from the test benches matched the expected outcomes.

### >> T flip flop testbench :

The simulation results demonstrate the functionality of the TFF module. The Q output toggles and the T input is asserted. When the T input is deserted, the Q output retains its current value. The reset signal is used to initialize the Q output to 0 at the start of the simulation.

Overall, the TFF module successfully exhibits the behavior of a toggle flip-flop circuit, as observed in the simulation results.

 


Figure 9: T-flip flop testbench simulation

```
° run 100 ns
° # KERNEL: At time 0, Q = x, reset = 1, T = 0
° # KERNEL: At time 10, Q =x, reset = 0, T= 0
° # KERNEL: At time 10, Q =0, reset = 0, T= 0
° # KERNEL: At time 15, Q =0, reset = 0, T= 1
° # KERNEL: At time 25, Q =0, reset = 0, T= 0
° # KERNEL: At time 30, Q =0, reset = 0, T= 1
° # KERNEL: At time 50, Q =0, reset = 0, T= 0
° # KERNEL: At time 65, Q =0, reset = 0, T= 1
° # RUNTIME: Info: RUNTIME 0068 Proj1210880.v (52): $finish called.
```

Figure 10: T-flip flop testbench result

## >>testbench module:

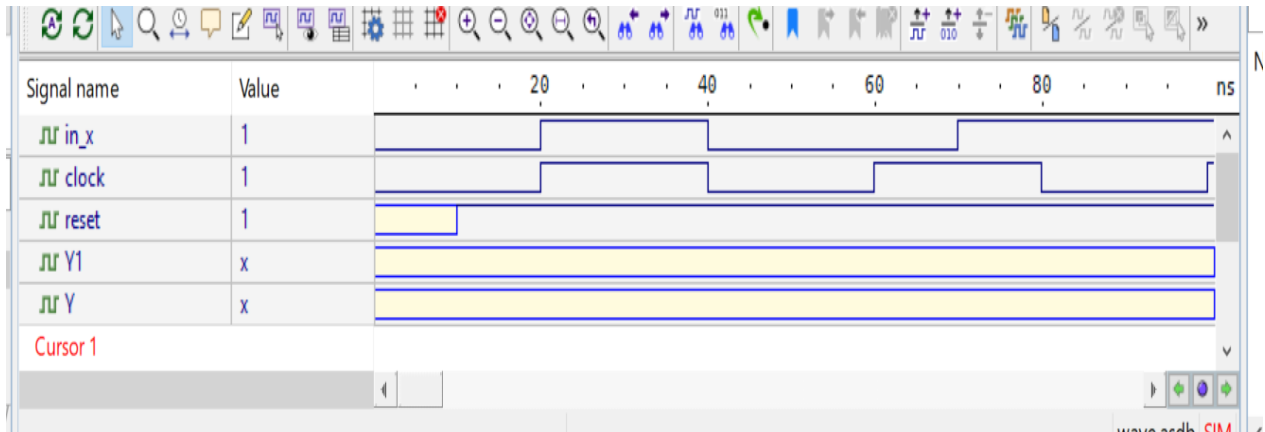


Figure 11: testbench module simulation

```
◦ # Waveform file 'untitled.awc' connected to 'c:/My_Designs/project1210880/proj1210880/src/wave.asdb'.
◦ run 100 ns
◦ # KERNEL: false
◦ # KERNEL: false
◦ # KERNEL: false
◦ # KERNEL: stopped at time: 100 ns
◦ run 100 ns
◦ # KERNEL: false
◦ # KERNEL: false
◦ # KERNEL: stopped at time: 200 ns
◦ run 100 ns
◦ # KERNEL: false
◦ # KERNEL: stopped at time: 300 ns
◦ # KERNEL: Simulation has finished. There are no more test vectors to simulate.
◦ run 100 ns
◦ # KERNEL: stopped at time: 400 ns
◦ # KERNEL: Simulation has finished. There are no more test vectors to simulate.
◦ run 100 ns
>
```

Figure 12: testbench module result

## Conclusion and Future work

In conclusion, this project successfully devised and executed a Moore Finite State Machine (FSM) for the precise detection of the "1011" sequence. This accomplishment was achieved through the strategic integration of T-Flip Flops and combinational logic, resulting in a highly efficient sequence detector. The effectiveness of the circuit was rigorously validated using a comprehensive testbench that meticulously compared the actual output to the expected output, reaffirming the circuit's reliability and correctness.

Regarding future enhancements, several promising avenues can be explored to further elevate the capabilities of the sequence detector circuit. Firstly, expanding the bit width of the detector registers can significantly extend its sequence detection capacity, allowing it to recognize more intricate patterns beyond "1011." This expansion would necessitate corresponding adjustments in storage and logic design to accommodate the increased complexity.

Furthermore, the circuit's versatility can be enhanced by enabling it to detect a broader spectrum of sequences or mathematical patterns. This endeavor would entail modifying the combinational logic and state transitions to cater to diverse detection criteria, thereby making the circuit adaptable to a wider range of applications.

Efficiency optimization remains a crucial aspect of future work. Evaluating alternative flip-flop types, such as D flip-flops or JK flip-flops, can offer insights into potential enhancements in terms of power efficiency and speed. Implementing advanced techniques like clock gating can effectively minimize power consumption, making the circuit more energy-efficient.

In summary, the sequence detector circuit, while currently adept at detecting the "1011" sequence, holds substantial potential for further development. By increasing its sequence detection capacity, diversifying its detection capabilities, and optimizing its efficiency, this circuit can evolve into a versatile and powerful tool suitable for a wide array of practical applications.

## APPENDIX CODE :

```
//1210880
//Sec:1
//T flip-flop module
module T_flipflop(Q,T,clock,reset);
    output Q;
    input T,clock,reset;
    reg Q;

    always@(posedge clock or negedge reset)
        if(~reset)
            Q=1'b0;
        else
            Q=Q^T;
endmodule
```

```
//Baraa Nasar
//1210880
//Sec:1
//T flip-flop Testbench module
module TFF_Testbench;
    reg clk, reset, T;
    wire Q;

    // Instantiate the T flip-flop module
    T_flipflop dff(Q, T, clk, reset);

    // Clock generation
    always begin
        #5 clk = ~clk;
    end

    // Initial block
    initial begin
        // Initialize signals
        clk = 0;
        reset = 0;
        T = 0;

        // Apply reset
        reset = 1;
```

```

#10 reset = 0;

#5 T = 1;
#10 T = 0;
#5 T = 1;
#20 T = 0;
#15 T = 1;
#30 T = 0;

// End simulation
$finish;
end

// Monitor block to display output
always @(Q,T,reset) begin

if (reset==1)
    $display ("At time %t, Q = x, reset = %b, T = %b", $time, reset, T);
else

    $display("At time %t, Q=%b, reset = %b, T= %b", $time, Q, reset, T);
end
endmodule

```

```

//Baraa Nasar
//1210880
//Sec:1
//structural circuit using T-Flip Flops
module SequenceDetector (
    input clock,
    input reset,
    input in_x,
    output reg Y1
);
    wire A,B,C,TA,TB,TC;

    or(TA,A,(B&C&in_x)); //TA=A+BCX

    or(TB,(A&~in_x),(B&~C&~in_x),(B&C&in_x),(~B&C&~in_x));

```



```
or(TC,(A&B),(C^in_x),(B&C&in_x));//TC=AB+C^X+BCX
```

```
T_flipflop G1( A,TA,clock,reset);  
T_flipflop G2( B,TB,clock,reset);  
T_flipflop G3( C,TC,clock,reset);  
assign Y1=A;
```

```
endmodule
```

```
//Baraa Nasar
```

```
//1210880
```

```
//Sec:1
```

```
//behavioural description of the circuit
```

```
module sqd_moore( output reg in_x, output reg clock, output reg reset, output reg Y);
```

```
initial begin
```

```
    in_x =0;
```

```
    clock =0;
```

```
    #10ns reset =1;
```

```
#10ns in_x=1;
```

```
#20ns in_x=0;
```

```
#30ns in_x=1;
```

```
#40ns in_x=1;
```

```
end
```

```
initial begin
```

```
repeat (11)
```

```
#20ns clock=~clock;
```

```
end
```

```
parameter S0=3'b000,
```

```
        S1=3'b001,
```

```
        S2=3'b011,
```

```
        S3=3'b010,
```

```
        S4=3'b110;
```

```
reg[1:0] Prsent_state,Next_state;
```

```
always @(posedge clock or negedge reset)
```

```
begin
```

```
if(reset==0)
```

```
    Prsent_state <= S0;
```

```

else
Prsent_state<=Next_state;
end
begin

always @(Prsent_state ,in_x)
begin
case (Prsent_state)
S0:begin
if(in_x==1)
Next_state <= S1;
else
Next_state <= S0;
end
S1:begin
if(in_x==0)
Next_state <=S2;
else
Next_state <=S1;
end
S2:begin
if(in_x==0)
Next_state <=S0;
else
Next_state <=S3;
end
S3:begin
if(in_x==0)
Next_state <=S2;
else
Next_state <=S4;
end
S4:begin
if(in_x==0)
Next_state <=S2;
else
Next_state <=S1;
end
endcase
end
always @(Prsent_state)
begin
case (Prsent_state)

```

```

S0: Y<=0;
S1: Y<=0;
S2: Y<=0;
S3: Y<=0;
S4: Y<=1;
endcase
end
end

```

```

endmodule

```

```

//Baraa Nasar
//1210880
//Sec:1
module testanalyser (clock, Y1 , Y);
input clock,Y1 , Y ;

```

```

always @(posedge clock) begin
if (Y1==Y)
    $display("True");
else
    $display("false");
end

```

```

endmodule

```

```

//Baraa Nasar
//1210880
//Sec:1
module testbench ;

```

```

wire in_x,clock,reset;
reg Y1 , Y ;

```

```

sqd_moore t1(in_x,clock,reset,Y);

```

```

    SequenceDetector t3(clock,reset,in_x,Y1);

```

```

testanalyser t2(clock, Y1 , Y);

```

```

endmodule

```